Series Circuit

Create a continuous pathway that can carry an electric current to light up a tiny bulb.

Place your LED here.
This is the LIGHT SOURCE.
Follow the directions on the next page to connect the LED.

Carefully cover grey lines with copper tape. The copper is a CONDUCTOR. It creates a pathway for the electric current.

Place battery here with the negative side facing down. The battery is the POWER SOURCE.


Fold on this line to make a SWITCH.
The switch opens and closes the circuit.






Attach the LED

(Light Emmitting Diode)

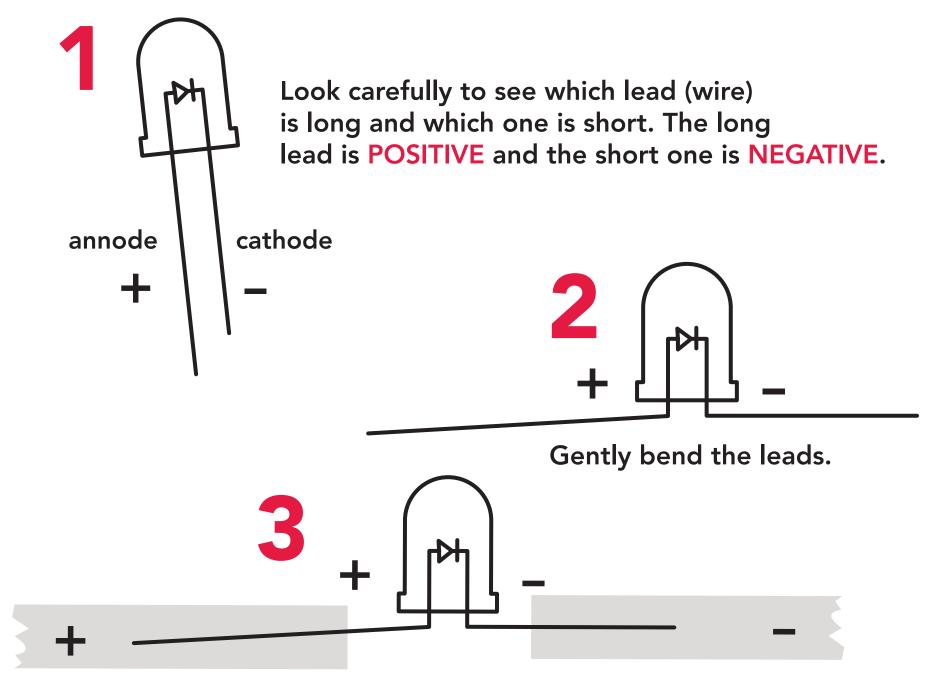

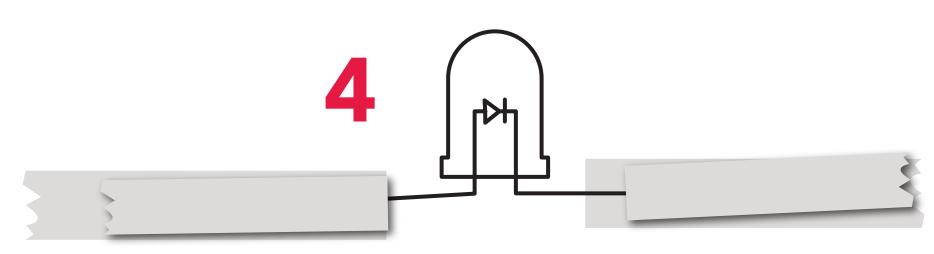Place the LED onto the copper tape. Be sure to match positive with positive and negative with negative.



Now cover the ends of the leads with little pieces of copper tape. Press the tape down very well.





WHAT CAN LIGHT UP?

car headlights lighthouse porch light stars cell phone robot train

camera flash lightbulb elevator buttons


WHAT WOULD LOOK **COOL WITH A LIGHT?**


gold tooth crazy eye diamond ring a good idea campfire super hero hurting finger Rudolph's nose piece of candy


WHAT ELSE?






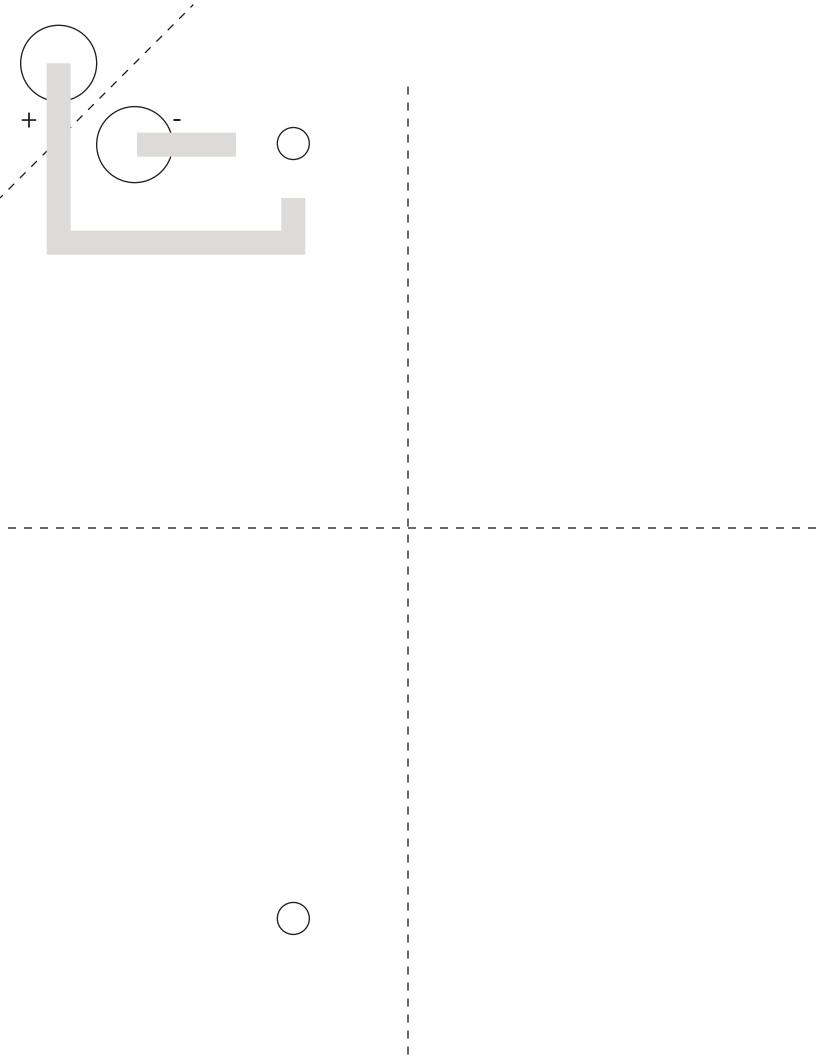

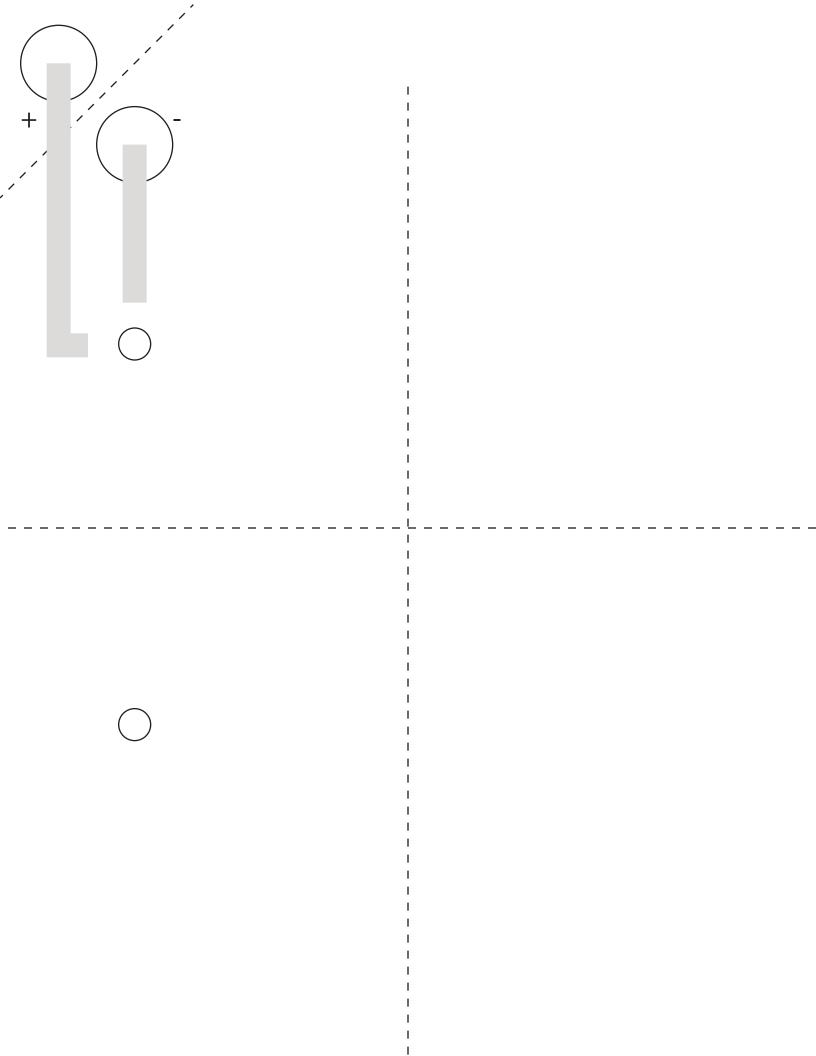

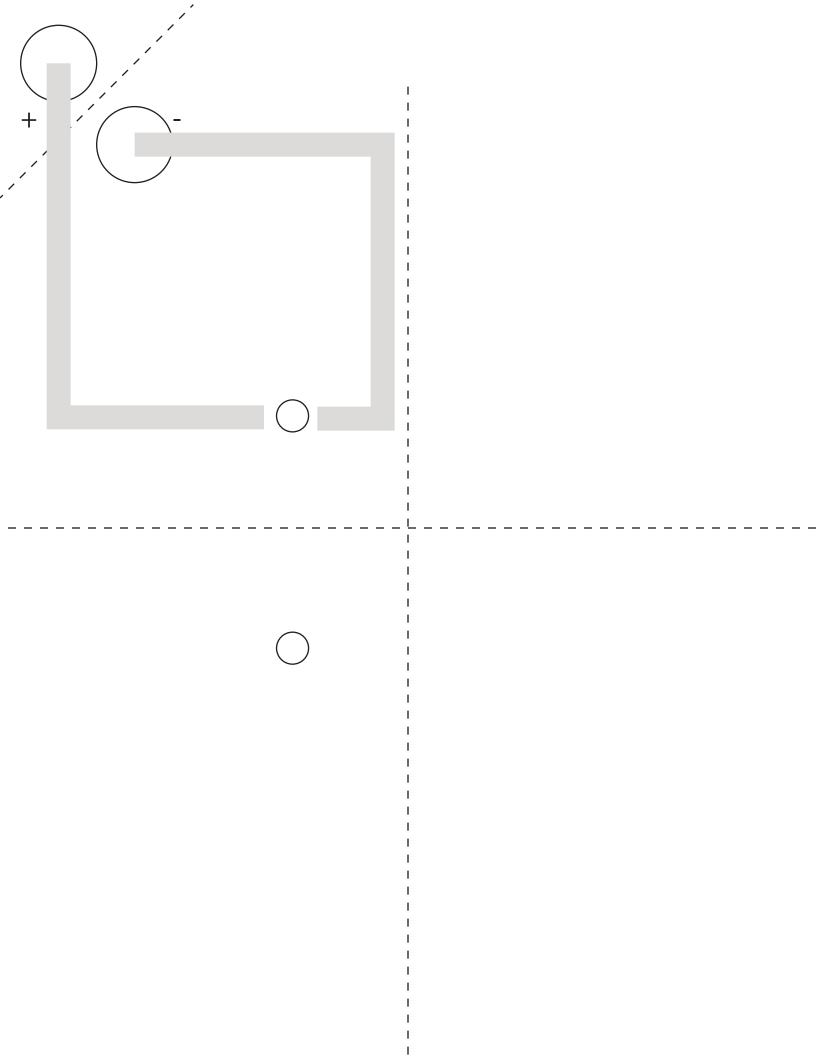

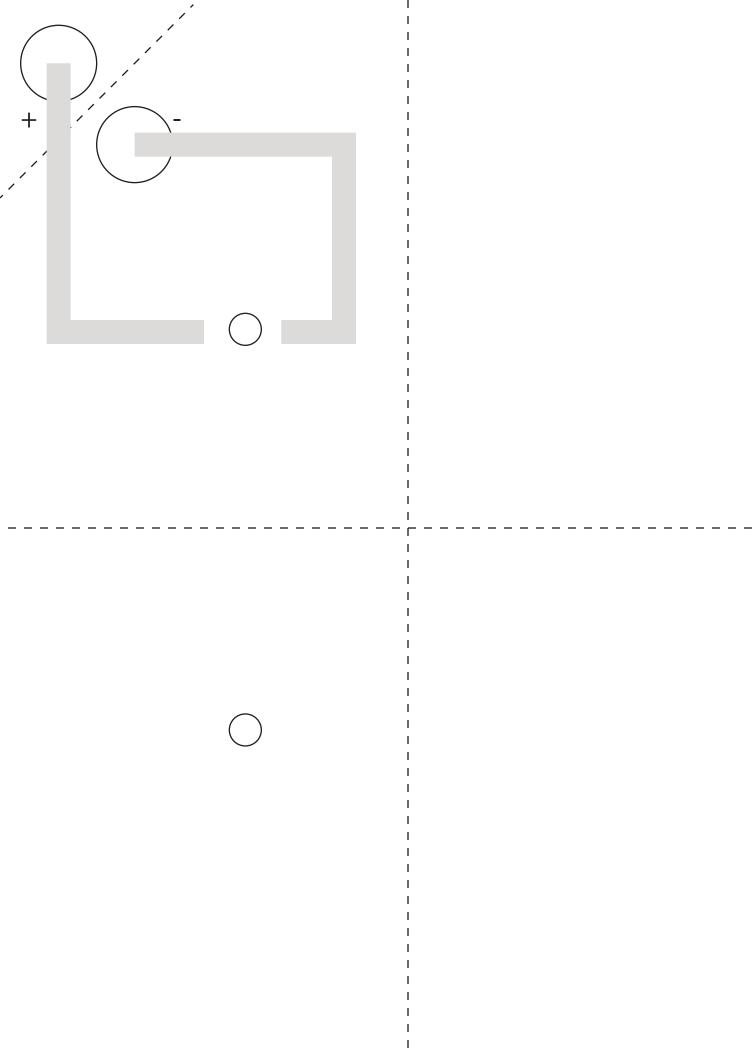

Copper Tape (55 yds) Conductive adhesive tape for making circuits	http://www.amazon.com/inch-yds-Copper-Foil -Tape/dp/B00CBPK0FW/ref=sr_1_3?ie=UTF 8&qid=1439156499&sr=8-3&keywords=copp er+tape
Box of <u>3V Coin Cell Batteries (100)</u> You need one battery per project	http://www.amazon.com/Maxell-CR2032-Lithi um-Battery-Batteries/dp/B001RID9ZM/ref=sr _1_2?ie=UTF8&qid=1432444678&sr=8-2&ke ywords=3V+coin+cell+battery
Packs of Small Binder Clips (144) To act as a switchholding the battery in place	http://www.amazon.com/Universal-Small-Bin der-Silver-10200VP/dp/B00B9GTBYA/ref=pd _sim_229_1?ie=UTF8&refRID=1KPY9VKGB T7VTSXTVFHK
White LEDs 5mm Avoid using the colored bulbs because they can use different amounts of energy	http://www.amazon.com/Bluecell-White-Electr onics-Ultra-Bright/dp/B005ONQ41W/ref=sr_1 _2?s=hi&ie=UTF8&qid=1447344949&sr=1-2 &keywords=5mm+white+LED
Sheet of Velostat One piece will go a long wayuse this to make the pressure sensitive fade switch	https://www.adafruit.com/products/1361
Colorful Transparent Sheets Totally optionalthis is great to diffuse the light into different colors	http://www.amazon.com/Hygloss-Cello-Sheet s-11-Inch-48-Pack/dp/B000K78HUI/ref=pd_si m_201_4?ie=UTF8&refRID=1912NWQ9CYG A2SMW1HY1
White Circuit Stickers These are more expensive but easier to usesurface mount LED stickers. Choose these OR the bulb LEDs	http://store.chibitronics.com/collections/all/products/white-leds-megapack-30-stickers